

Cork Institute of Technology

Higher Certificate in Engineering in Electrical Engineering-Award

(NFQ Level 6)

Autumn 2006

Electrical Engineering

(Time: 3 Hours)

Attempt **Five** Questions


Examiners: Mr. J. Hurley
Mr. M. Hennessy
Prof. E. McQuade

1. (a) An impedance of $(3-j4) \Omega$ is connected in parallel with an impedance of $(8+j6) \Omega$ across a 20 V supply. Calculate the magnitude and power factor of the current taken from the supply. (8 marks)
- (b) A 230 V single phase supply has the following loads: (i) incandescent lamps taking a current of 8 A at a power factor of 1.0; (ii) fluorescent lamps taking a current of 12 A at a power factor of 0.6 lagging; (iii) a motor load of 8 A at a power factor of 0.8 lagging. Calculate the total supply current and the power factor. (8 marks)
- (c) What is the total power taken from the supply? (4 marks)

2. (a) State the numerical relationship between line and phase voltages and currents in a three-phase delta-connected load. (4 marks)
- (b) Three coils are connected in delta to a three-phase, three wire, 400-V, 50-Hz, supply and take a line current of 10A at 0.8 power factor leading. Calculate the resistance and inductance of each coil. (10marks)
- (c) If the coils are now connected in star across the same supply, calculate the line current and the power. (6 marks)

3. (a) Why is the three-phase four wire distribution normally used for A.C. distribution?(3 marks)
- (b) A three-phase 400 V system four-wire system has the following single-phase loads:
Red phase 6 kW at 0.9 power-factor lagging,
Yellow phase 3 kW at 0.7 power factor lagging,
Blue phase 9 kW at 0.8 power factor lagging.
Calculate the current in each line and the neutral current.
Assume the phase sequence to be R Y B (17 marks)

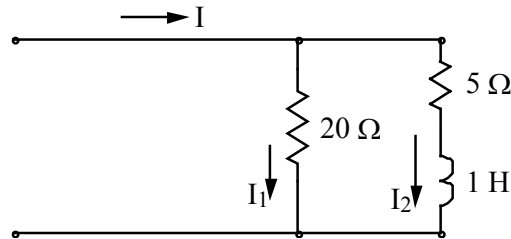4. (a) Define the time-constant as applied to a circuit consisting of a resistance and an inductance connected in series. (3 marks)
- (b) In the circuit shown the supply is 5 V D.C. and is applied to the circuit at time $t = 0$. Find the values of the currents I , I_1 and I_2 under final steady state conditions. Find also the time constant of the inductive branch and the value of each current after 0.1 s. (17 marks)



5. (a) Explain with a circuit diagram how the open-circuit test is performed on a single phase transformer. What information can be got from the open-circuit test? (5 marks)
- (b) A single-phase transformer is rated at 1.8 kVA, 240 V/120 V. When the secondary terminals are open-circuited and the primary winding is supplied at normal voltage (240 V), the power taken is 20 W. When the secondary terminals are short-circuited, the power required to circulate full load current in the short-circuited secondary is 35 W. Calculate: (a) the efficiency of the transformer at full load, 0.8 power factor lagging; (b) the load at which maximum efficiency occurs. (15 marks)
6. (a) Explain how a rotating magnetic field is produced in a three-phase induction motor. (5 marks)
- (b) The power input to a four-pole, three-phase, 50-Hz, induction motor is 64 kW; the speed is 1470 rev/min. The stator losses are 1.2 kW and the friction and windage losses are 2.0 kW. Find (i) the slip; (ii) the output power; (iii) the rotor copper loss; (iv) the efficiency. (15 marks)
7. (a) Sketch the torque speed characteristic for a series type d.c. motor. What precautions should be taken when using this type of motor? (6 marks)
- (b) A series motor takes a current of 2 A from a 400 V d.c. supply and runs at 2,500 rev/min on light load. When the motor is loaded it takes 40 A from the same supply. Calculate the full load speed of the motor. The resistances of the armature and of the series field are 0.2 Ω and 0.1 Ω respectively. Assume that the flux is proportional to the field current and ignore the effects of armature reaction. (14 marks)

Useful Formulae

$$\text{Capacitive Reactance} \quad X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{-j}{\omega C} = \frac{1}{j\omega C} \quad (\Omega)$$

$$\text{Inductive Reactance} \quad X_L = \omega L = 2\pi f L = j\omega L \quad (\Omega)$$

Series Circuit

$$\text{Impedance} \quad Z = \sqrt{R^2 + (X_L - X_C)^2} \quad (\Omega)$$

$$\cos\theta = \frac{R}{Z}$$

Parallel Circuit

$$\text{Two Impedances in Parallel} \quad Z_T = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

Only when Z_1 and Z_2 are expressed in complex form.

$$\text{Time Constant} \quad T = \frac{L}{R} \quad (\text{s})$$

Growth of Current in a RL circuit

$$i = \frac{V}{R} \left\{ 1 - e^{-\frac{Rt}{L}} \right\} \quad (\text{A})$$

$$\text{Voltage across inductance} \quad v_L = V \left\{ e^{-\frac{Rt}{L}} \right\} \quad (\text{V})$$

Three-Phase Star Connection

$$V_{Line} = \sqrt{3} V_{Phase}$$

$$I_{Line} = I_{Phase}$$

$$\text{Power in Balanced Load} \quad P = \sqrt{3} V_L I_L \cos\theta \quad (\text{W})$$

Three-Phase Delta Connection

$$V_{Line} = V_{Phase}$$

$$I_{Line} = \sqrt{3} I_{Phase}$$

$$\text{Power in Balanced Load} \quad P = \sqrt{3} V_L I_L \cos\theta \quad (\text{W})$$

$$\text{Unbalanced Load} \quad P_T = P_1 + P_2 + P_3 \quad (\text{W})$$

$$\text{Power Factor Correction} \quad \text{Cap. kVAr} = kW (\tan\theta_2 - \tan\theta_1)$$

$$\text{Power Factor} = \frac{\text{True Power}}{\text{Apparent Power}}$$

$$\text{Reactive Power} = VI \sin\theta \quad (\text{VAr})$$

$$\text{True Power} = VI \cos\theta \quad (\text{W})$$

$$\text{Apparent Power} = VI \quad (\text{VA})$$

$$\text{Ideal Transformer} \quad \frac{V_P}{V_S} = \frac{N_P}{N_S} = \frac{I_S}{I_P}$$

$$\text{Approximate Volt Drop} \quad I_P \bar{R}_P \cos\theta \pm I_P \bar{X}_P \sin\theta \quad (\text{V})$$

$$\text{Per Unit Regulation} \quad \frac{V_{NL} - V_{FL}}{V_{NL}}$$

$$\frac{\text{Approximate Volt Drop}}{V_p} \times 100\% \quad (\%)$$

Synchronous speed $N_s = 60f/p$ (r/min)

f = frequency

p = pairs of poles

Per Unit Slip $s = \frac{N_s - N_r}{N_s}$

Rotor Speed $N_r = N_s(1 - s)$ (r/min)

Rotor Frequency $f_r = sf$

DC Machines

D.C. Motor

$$E_b = V - I_a R \quad (\text{V})$$

$$N = K \frac{V - I_a R}{\phi} \quad (\text{r/min})$$

$$E_b = KN\phi$$