

# Cork Institute of Technology

## Higher Certificate in Engineering in Electrical Engineering – Award

(NFQ Level 6)

Autumn 2006

### Electrical Power Systems & Equipment

(Time: 3 Hours)

Instructions  
Answer FIVE questions.  
All questions carry equal marks

Examiners: Mr. J. C. Duggan  
Mr. M. Hennessy  
Prof. E. McQuade

- Q1. The start-up sequence for an industrial plant is specified below. Control is by single stop and start push buttons. Motors  $M_1$ ,  $M_2$  and  $M_3$  are to be started in sequence with 10s intervals between each start.
- After  $M_3$  has started a solenoid valve,  $SV_1$ , is to operate for 1 minute and then turn off. An O/L on any motor stops all. An emergency stop is required. Develop a suitable control circuit. (20 marks)
- Q2. (a) A 400V, 50Hz industrial supply has an impedance of  $0.0013 + j 0.0061\Omega$ . Cables from transformer to L.T bus-bars have a resistance of  $0.15m\Omega$ . A balanced three phase short-circuit occurs on the bus-bars.
- Using the information supplied in appendix A and diagrams 3 or 4 determine
- (i) The steady state RMS symmetrical current.
  - (ii) The initial peak asymmetrical current.
- Take the value of E as 410 and F as 1.1 (10 marks)
- (b) A H.T supply has a capacity of 20 MVA and a  $Z_{pu}$  of 0.25. Two transformers  $T_1$  and  $T_2$  are supplied from this source.  $T_1$  and  $T_2$  are identical and have values of 6 MVA and  $Z_{pu}$  of 0.05.
- Determine the maximum fault level when the transformers are connected in parallel. (10 marks)

- Q3. (a) Equipment for use in potentially explosive gas atmospheres is classified in terms of suitability for
- (i) Gas Groups.
  - (ii) Hazardous Areas.
  - (iii) Temperature Class.
- Explain the significance of each. (9 marks)
- (b) A squirrel cage induction motor intended for use in a potentially explosive gas atmosphere has part of its marking labelled as EEx 'd,e'.
- Explain the principle of the protection method(s) provided by this motor. (6 marks)
- (c) Write a brief note on the ATEX directives. (5 marks)
- 
- Q4. (a) Describe a moulded case circuit breaker (MCCB). (5 marks)
- (b) State the advantages of using solid state (electronic) trip units in MCCBs. (5 marks)
- (c) Outline the arrangements of switch contacts in an MCCB to facilitate
- (i) Conduction of current.
  - (ii) Making and breaking of current. (5 marks)
- (d) A *reverse loop* magnetic blow-apart contact system is often used in MCCBs. Briefly describe how this system works. (5 marks)
- 
- Q5. (a) Describe the construction of
- (i) A standard rotor of a squirrel cage induction motor (SCIM)
  - (ii) The rotor of a double cage or high torque SCIM. (8 marks)
- (b) Sketch and explain the speed / torque characteristic of the motors in (a) above. (6 marks)
- (c) Describe the arrangements for starting a wound rotor induction motor (WRIM). Explain how the rotor of such a motor produces an increased torque during starting conditions. (8 marks)

- Q6. (a) Write a concise note to explain why reduced voltage starting methods may sometimes be required for SCIM. (6 marks)
- (b) List *four* such starting methods. (4 marks)
- (c) Sketch the power (mains) circuit for a star-delta starter. (6 marks)
- (d) Explain a delta-loop star-delta starter and state its advantage. (4 marks)
- Q7. (a) Describe how an inductor motor may be protected against
- (i) Short Circuit. (6 marks)
- (ii) Overload. (6 marks)
- (b) A SCIM requires a long run-up time when starting against a load known to have a high inertia. Describe a method of overload protection which may be applied to such a starting condition. (8 marks)
- (c) What is meant by the term “single phasing” as applied to a three phase motor? What arrangements are made against this condition causing stator burn-out? (6 marks)
- Q8. (a) For an ACB or MCCB what is meant by the following
- (i) Rated current,  $I_N$
- (ii) Frame size rating.
- (iii) Rated ultimate breaking capacity,  $I_{CU}$
- (iv) Rated short-time withstand current,  $I_{CW}$
- (v) Rated insulation voltage,  $U_i$  (10 marks)
- (b) The supply arrangements to an industry requires that a number of circuit breakers may only be closed in a defined way.
- Breakers  $C_1$  and  $C_2$  may be closed together.
- Breaker  $C_3$  may be closed in combination with either  $C_1$  or  $C_2$ , *but not both*.
- Describe a key interlocking system to facilitate this. (6 marks)
- (c) Distinguish between a “short key” and a key exchange box system of Cartell interlocks. (4 marks)

4.3

### RELATIONSHIP BETWEEN SUPPLY SYSTEM SHORT-CIRCUIT VALUES

The short-circuit current values  $I_p$ ,  $I_s$  and  $I_k$  described in 4.1, and shown in Diagram 1 are related as follows:

$$I_k = \frac{V_r}{\sqrt{3} \times Z} \times 1.1^*$$

$$I_s = I_k + \text{contribution from connected motors (See 4.2 above).}$$

$$I_p = I_s \times M$$

Where  $V_r$  = rated line voltage (RMS) of the transformer.

$Z$  = impedance to point of fault in ohms.

\*1.1 is a factor to take account of high voltage value on the HV side.

$M$  = Asymmetry factor which is a function of the  $\frac{R}{X}$  ratio of the faulted circuit. (See Diagram 3).

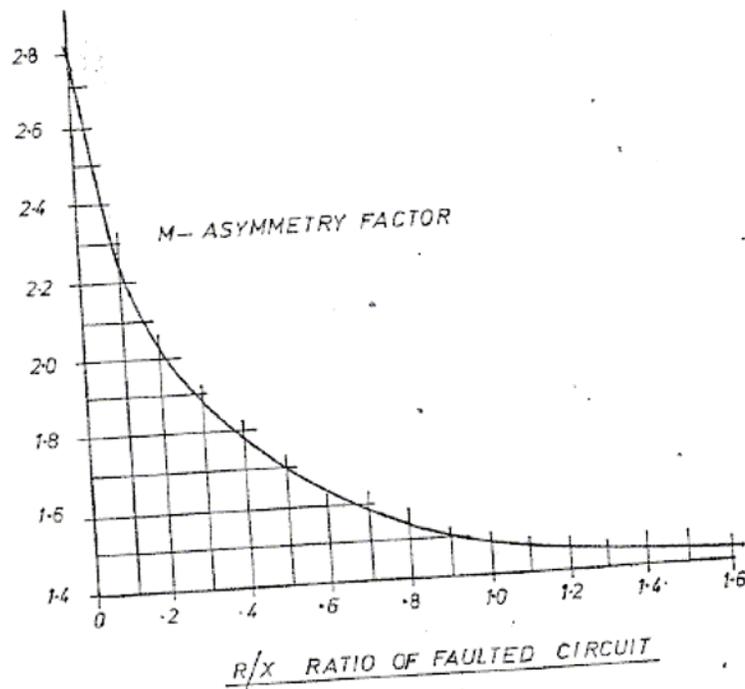


Diagram 3.

APPENDIX A

EXAMPLES OF FAULT LEVEL CALCULATIONS

A-1

**METHODS OF CALCULATING SHORT CIRCUIT VALUES**

The following formulae are applicable to the calculation of the short circuit values defined in Section 4.

(a) Steady State Symmetrical Short Circuit Current.

$$I_k = \frac{E \times F}{\sqrt{3} \times Z} (A+jB) \text{ in RMS Amps}$$

$$I_k = \text{Absolute value of } I_k \text{ in RMS Amps.}$$

(b) Initial Symmetrical Short Circuit Current.

$$I_s = I_k + I_m \text{ (RMS Amps.)}$$

$$I_s = \text{Absolute Value of } I_s \text{ in RMS Amps.}$$

(c) Peak Asymmetrical Short Circuit Current.

$$I_p = I_s \times M \text{ (Instantaneous Amps.)}$$

Where

$$E = \text{Circuit EMF in Volts.}$$

$$= \text{Rated 10 kV/LV transformer open-circuit voltage.}$$

$$F = \text{Factor to allow for tap ratio, and H.V. system voltage variations.}$$

$$Z = \text{Absolute Value of total circuit impedance in ohms.}$$

$$A+jB = \text{Cosine and Sine of phase angle of } I_k \text{ with respect to } E.$$

$$A = R / \sqrt{R^2 + X^2}$$

$$B = X / \sqrt{R^2 + X^2}$$

$$R = \text{Total Resistance of impedance of Figure 4.2 ohms.}$$

$$X = \text{Total Reactance of impedance of Figure 4.2 ohms.}$$

(Note: These circuits are generally inductive, and in such cases B is negative).

$$I_m = \text{Motor short circuit current.}$$

$$= 6 \times (\text{Motor Rated Current}) \times (0.3 - j0.954)$$

If the motor rated current is not known, it should be assumed equal to the transformer rated current.

$$M = \text{The asymmetry factor which is a function of the R/X ratio of the faulted circuit. It may be read from Diagram 3.}$$

Examples of calculations are given in Appendix A-2, and data for some frequently occurring applications are given in Appendix A-3.

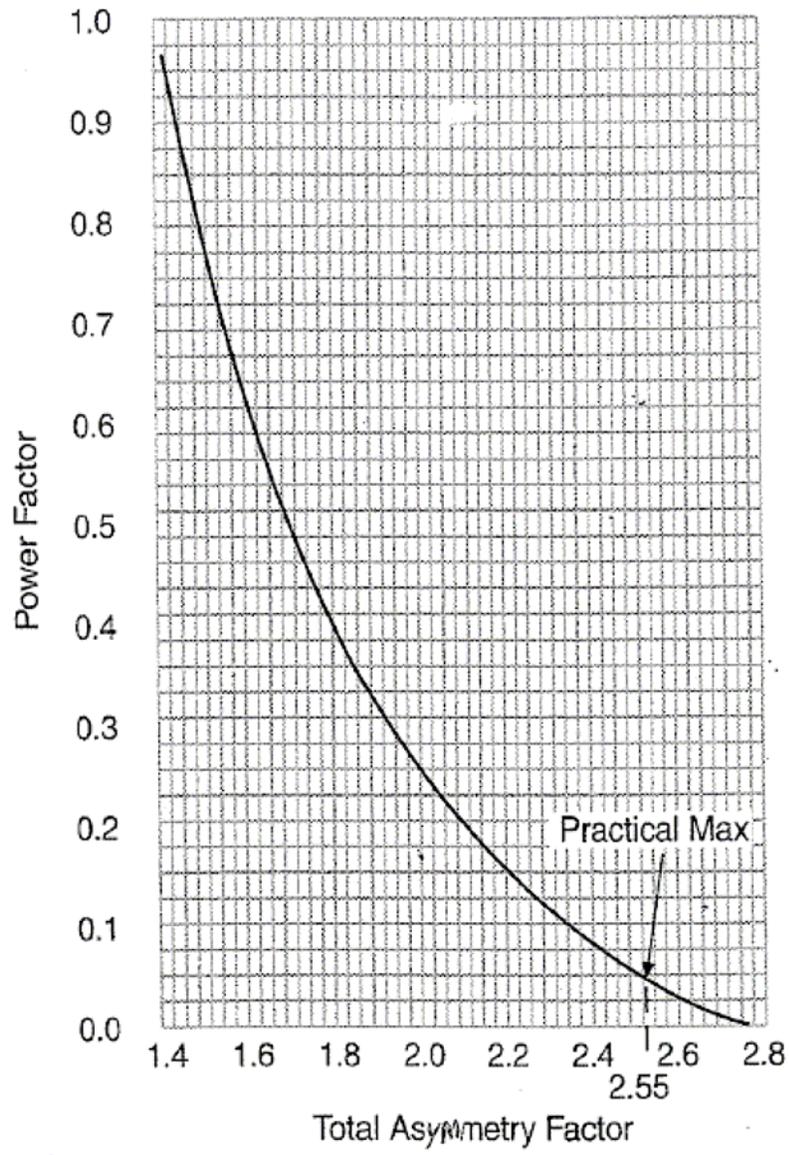


Figure 4  
Asymmetry Factor Chart