

# Cork Institute of Technology

Higher Certificate in Engineering in Electrical Engineering – Award

(NFQ Level 6)

Summer 2007

## Electrical Power Systems & Equipment

(Time: 3 Hours)

Instructions  
Answer **FIVE** questions.  
All questions carry equal marks.

Examiners: Mr. J. C. Duggan  
Mr. M. Hennessy  
Prof. E McQuade

- Q1. (a) With the aid of neat labelled sketches, explain the following types of short circuit faults.
- (i) three-phase balanced fault
  - (ii) ungrounded phase to phase fault
  - (iii) phase to ground fault (6 marks)
- (b) A low voltage supply has a source impedance of  $0.0013 + j 0.0061 \Omega$ .  
The feed from transformer to LV bus-bars has a cable resistance of  $0.15 \text{ m } \Omega$ .  
A symmetrical (balanced) three-phase short circuit occurs across the bus-bars.  
Assuming values for voltage of 410 V and voltage variation of 1.1 and using tables supplied, calculate:
- (i) the final steady state symmetrical fault current
  - (ii) the initial asymmetrical peak fault current (10 marks)
- (c) Discuss the possible effects large motors installed close to the intake may have on the initial fault current cycles. (4 marks)
- Q2. (a) Outline the conditions necessary to allow two power transformers to operate in parallel. (5 marks)
- (b) The supply to an industry is obtained from two transformers connected in parallel.  
The load delivered is 500 kW at a power factor of 0.82, lag.  
Transformer  $T_1$  has resistance and inductive reactance values of 3.0 and  $4.5 \Omega$  respectively. The corresponding values for  $T_2$  are 2.8 and  $5.2 \Omega$ .  
Determine:
- (i) the power share in kW of each transformer
  - (ii) the power factor at which each transformer operates (15 marks)

Q3. (a) Identify the conditions necessary to cause an atmospheric explosion of a flammable substance. (3 marks)

(b) The nameplate on an apparatus intended for installation in a potentially explosive atmosphere includes the following markings:

Ex “1<sub>a</sub>” IIc T<sub>6</sub>

Explain the meaning of the codes used on this nameplate. (4 marks)

(c) Potentially Explosive Gas Atmospheres are defined by three terms:

(i) Gas Groups

(ii) Hazardous Zones

(iii) Temperature Classes

Explain the significance of each of these terms. (6 marks)

(d) Outline the principle of operation and give a practical application of one of the following protection methods:

(i) Ex, d

(ii) Ex, e

(iii) Ex, p (7 marks)

Q4. (a) Explain the concept of an intrinsically safe system. (4 marks)

(b) In relation to an intrinsically safe *associated apparatus*, explain:

(i) a non-countable fault

(ii) a countable fault

(iii) an infallible component (6 marks)

(c) For an intrinsically safe system, distinguish between:

(i) the ratings “1<sub>a</sub>” and “1<sub>b</sub>”

(ii) an IS *apparatus* and an IS *associated apparatus* (10 marks)

- Q5. (a) In relation to circuit breakers to IEC 947-2 (EN 60947-2), explain what is meant by:
- (i)  $I_{cm}$  , rated s/c making current
  - (ii)  $I_{cu}$  , rated ultimate breaking current
  - (iii)  $I_{cw}$  , rated short-time withstand current
  - (iv) Category A
  - (v) Category B
- (10 marks)
- (b) Briefly discuss *discrimination* and *cascading* for series connected (major and minor) LV circuit breakers. (5 marks)
- (c) Sketch the *general shape* of the trip characteristic of a LV circuit breaker. Explain the advantages of an electronic trip unit of a circuit breaker. (5 marks)
- Q6. (a) State concisely why squirrel cage induction motors (SCIM) are favoured as industrial drives. (5 marks)
- (b) With the aid of neat labelled sketches, show that you understand the concept, construction and application of:
- (i) a standard SCIM
  - (ii) a double cage SCIM
  - (iii) a wound rotor induction motor
- (15 marks)
- Q7. (a) For a typical induction motor, sketch:
- (i) the torque/speed curve
  - (ii) the current/speed curve
- (4 marks)
- (b) Explain why a reduced voltage starting method may sometimes be required for a squirrel cage induction motor (SCIM). (6 marks)
- (c) With the aid of a power (line) diagram, explain the operation of one method of reduced voltage starting of a SCIM. (10 marks)
- OR**
- (c) Briefly discuss the concept of soft starting for SCIM. (10 marks)

- Q8. (a) The LV supply to an industry is delivered from a supply company source which has a capacity of 15 MVA at a per unit impedance of 0.30.  
Two on-site transformers are fed from this supply.  
The rating of  $T_1$  is 5.5 MVA at 2 p.u. of 0.06, while  $T_2$  has a rating of 6 MVA at Z pu. of 0.05.  
Determine the fault level in MVA if the installation is fed from:
- (i)  $T_1$  only
  - (ii)  $T_2$  only
  - (iii)  $T_1$  and  $T_2$  connected in parallel (12 marks)
- (b) The supply arrangements for a factory requires that a number of circuit breakers may only be closed in a defined manner.  
 $CB_1$  and  $CB_2$  may be closed together.  
 $CB_3$  may be closed if  $CB_1$ , or  $CB_2$ , is closed but not with both  $CB_1$  and  $CB_2$  closed.  
Describe a suitable key interlocking system for this arrangement. (5 marks)
- (c) Discuss the advantages of a key-exchange box interlocking (Costell) system. (3 marks)

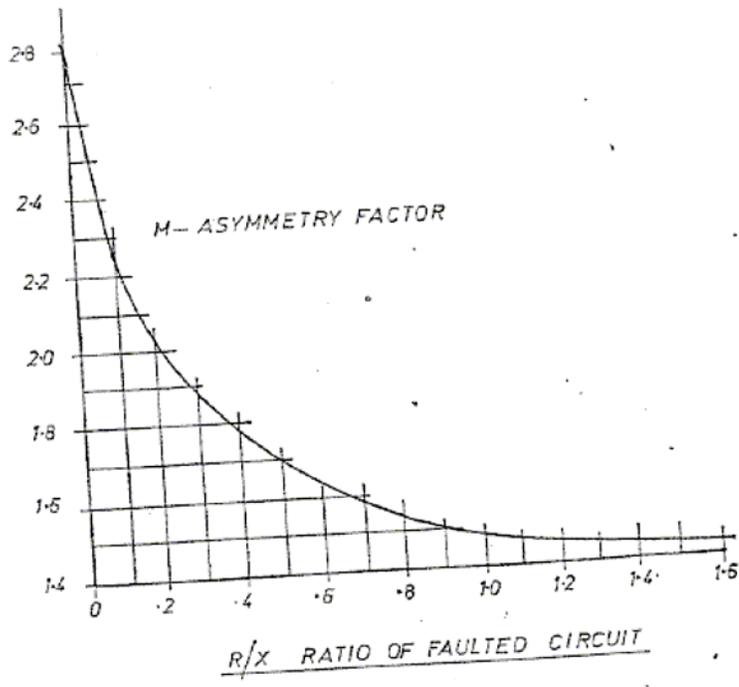


Diagram 3.

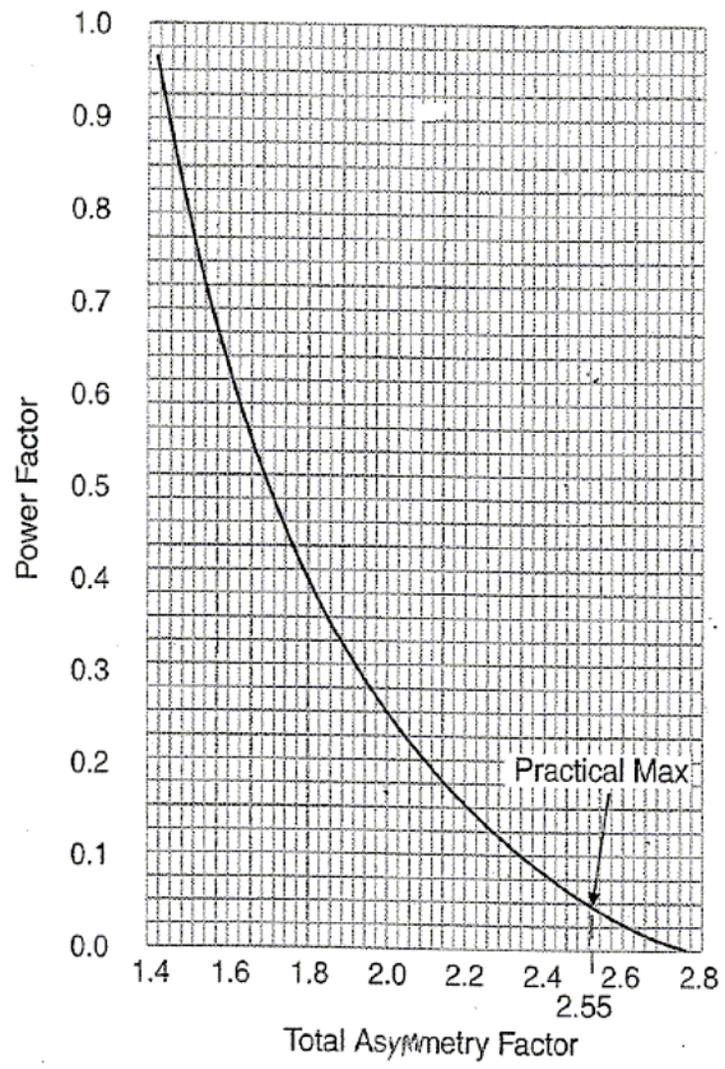


Figure 4  
Asymmetry Factor Chart

APPENDIX A

EXAMPLES OF FAULT LEVEL CALCULATIONS

A-1

**METHODS OF CALCULATING SHORT CIRCUIT VALUES**

The following formulae are applicable to the calculation of the short circuit values defined in Section 4.

(a) Steady State Symmetrical Short Circuit Current.

$$I_k = \frac{E \times F}{\sqrt{3} \times Z} (A + jB) \text{ in RMS Amps}$$

$$I_k = \text{Absolute value of } I_k \text{ in RMS Amps.}$$

(b) Initial Symmetrical Short Circuit Current.

$$I_s = I_k + I_m \text{ (RMS Amps.)}$$

$$I_s = \text{Absolute Value of } I_s \text{ in RMS Amps.}$$

(c) Peak Asymmetrical Short Circuit Current.

$$I_p = I_s \times M \text{ (Instantaneous Amps.)}$$

Where

E = Circuit EMF in Volts.  
= Rated 10 kV/LV transformer open-circuit voltage.

F = Factor to allow for tap ratio, and H.V. system voltage variations.

Z = Absolute Value of total circuit impedance in ohms.

A + jB = Cosine and Sine of phase angle of  $I_k$  with respect to E.

$$A = R / \sqrt{R^2 + X^2}$$

$$B = X / \sqrt{R^2 + X^2}$$

R = Total Resistance of impedance of Figure 4.2 ohms.

X = Total Reactance of impedance of Figure 4.2 ohms.

[Note: These circuits are generally inductive, and in such cases B is negative].

$I_m$  = Motor short circuit current.

$$= 6 \times (\text{Motor Rated Current}) \times (0.3 - j0.954)$$

If the motor rated current is not known, it should be assumed equal to the transformer rated current.

M = The asymmetry factor which is a function of the R/X ratio of the faulted circuit. It may be read from Diagram 3.

Examples of calculations are given in Appendix A-2 and data for some frequently occurring applications are given in Appendix A-3.